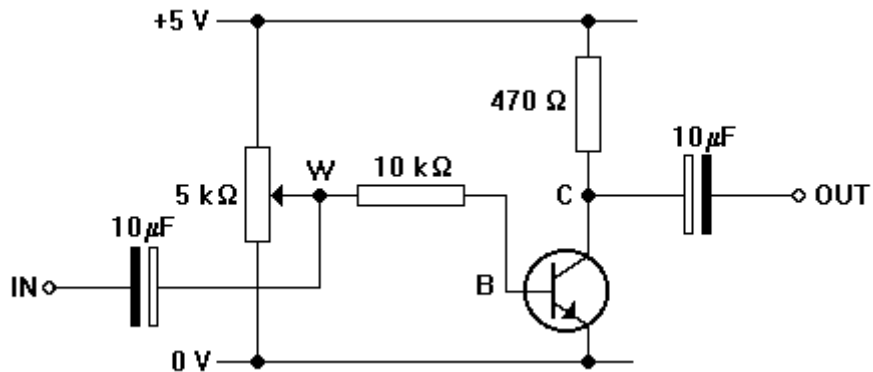


Investigating a common-emitter amplifier


- 1 Assemble the amplifier circuit shown below. Use a low power signal bipolar transistor.



- 2 Use a double-beam oscilloscope to monitor the voltages at W and C. If all is well, the voltage at C should fall as the voltage at W rises.
- 3 Set W to 0 V and slowly increase it until C starts to fall below +5 V. Note the value of the voltage at W. Then continue to increase the voltage at W until C hits 0 V and the transistor saturates. Note the new voltage at W.
- 4 Use the data from step 3 to calculate a value for the voltage gain of the circuit. Don't forget the sign.
- 5 Adjust the potentiometer so that C sits at +2.5 V. This should give the amplifier optimum bias.
- 6 Use a signal generator to feed a 1 kHz sine wave with a peak value of 200 mV into the amplifier. Trigger the oscilloscope on the signal at the output. Sketch waveforms of the signals at IN, W, B, C and OUT. Don't forget to show the scales of the voltage and time axes.
- 7 Use the peak values of the input and output waveforms to calculate a value for the voltage gain. How does it compare with your value calculated in step 4?
- 8 Investigate the effect on the output waveform of altering the d.c. voltage at W.
- 9 Return the bias to its original optimum setting (step 5). Without altering anything else, note what happens when you replace your transistor with different ones.

Electronics Explained: Transistor Circuits

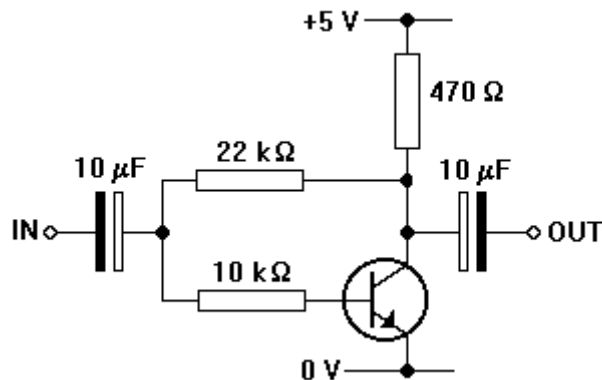- 10 Insert the original transistor. Remove the potentiometer. Use a 22 k resistor to provide bias from the collector, as shown below.



- 11 Measure the voltage gain of your new amplifier.
- 12 Note what happens now to the voltage gain and the bias if you replace the transistor with others.