

Introduction

There are many applications that require the synthesis of frequencies above 3 GHz. However, this range is generally beyond the maximum frequency that PLL devices can directly accept. By using an external prescaler, the range of a PLL can be extended. This Application Note explains how the PE3501 Divide-by-2 Prescaler can be used in combination with a PE3236 PLL to synthesize frequencies as high as 3.5 GHz.

Setup

Figure 1 shows the block diagram of the PE3501 and PE3236 used together in a high-frequency synthesizer. The PE3236 phase detector outputs are fed through a loop filter into a differential operational amplifier (see Figure 2). The voltage output of the op-amp is used to control the tuning pin of the voltage-controlled oscillator (VCO). The VCO used is capable of generating 3.0 to 3.5 GHz. A small portion of this VCO signal is fed back to the PE3501 prescaler input, where its frequency is divided in half. The resulting 1.50 to 1.75 GHz signal is then applied to the PE3236 frequency input. This is well below the upper frequency limit of 2.2 GHz for the PE3236.

Using the PE3501 Prescaler with the PE3236 PLL to Synthesize Frequencies up to 3.5 GHz

Features

- Extends F_{MAX} of available PLL devices
- Negligible additive phase noise
- Low power prescaler operation (12 mA @ 3V typical)

Figure 1. Block Diagram of PE3236 / PE3501 Loop


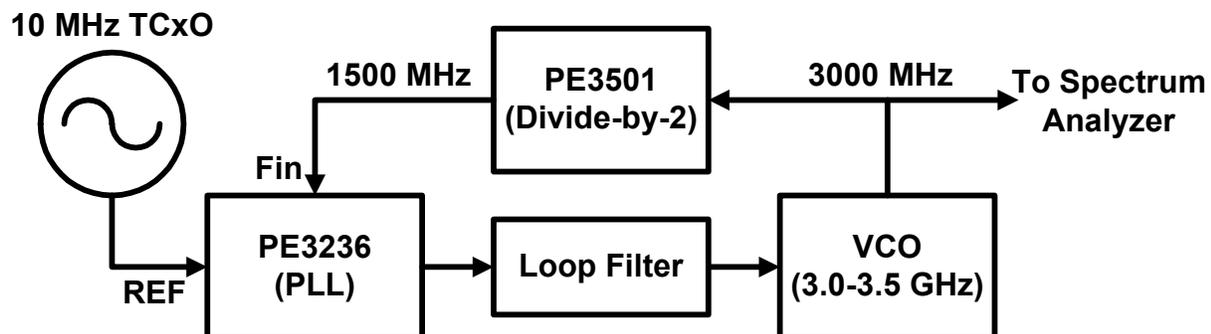


Figure 2. Loop Filter Used for This Design

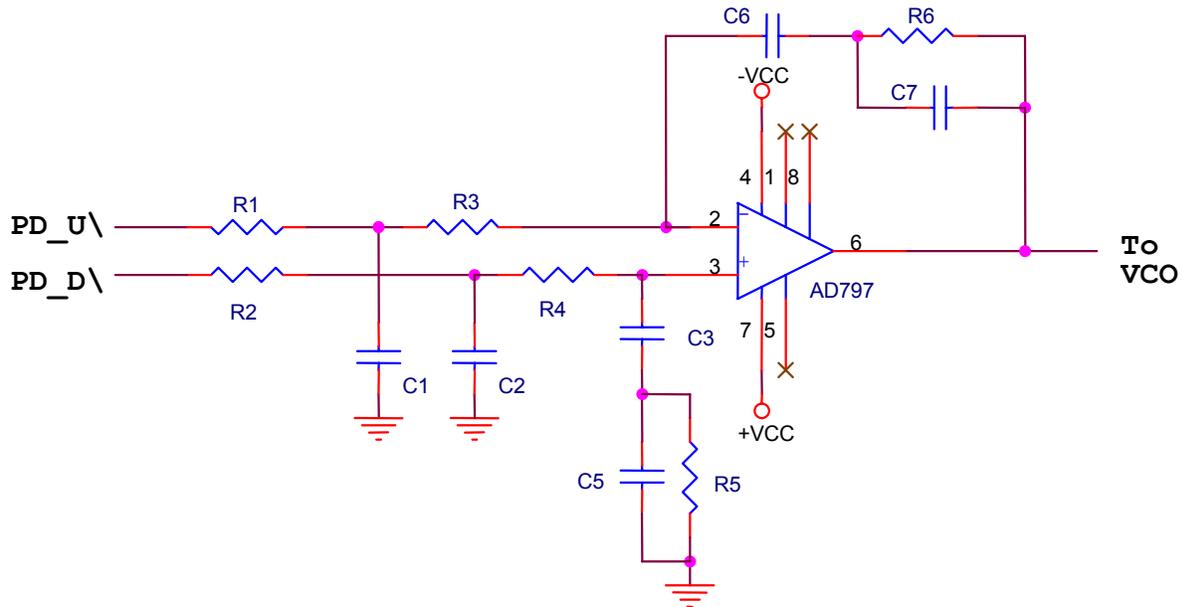

Loop Filter Setup:

In order to calculate the loop filter component values, several constants are needed. The following list represents those constants. Table 1 shows the calculated values for the loop filter components.

LPF Constants:

- VCO = Micronetics M3500C-2032S
- $K_{vco} = 100 \text{ MHz / V at } 3.0 \text{ GHz}$
- REF = Vectron TCXO OSC-3A0-10 MHz
- $F_c = 1 \text{ MHz}$
- Phase Detector Gain = 430 mV / RAD
- $R_1 = R_2 = 120 \text{ ohms}$
- $R_3 = R_4 = 390 \text{ ohms}$
- $C_5 = C_7 = 22 \text{ pF}$

Table 1. Loop Filter Parameters

LPF Characteristics		LPF Components		
BW (kHz)	Phase Margin (Degrees)	C1, C2	C3, C6	R5, R6
68.00	66.00	5.6 nF	4.7 nF	2.7 kohms

Results

Figure 3 shows the phase noise as measured at both the output of the VCO and the output of the PE3501 prescaler. In addition to these two plots, a third plot is shown which is exactly 6 dB below the VCO's phase noise plot. This third plot represents the theoretical phase noise improvement that results from dividing the VCO output frequency by 2. ($6 \text{ dB} = 20 \log(N)$, where N is the prescaler division ratio of 2).

We see from Figure 3 that this theoretical phase noise plot is almost identical to the actual phase noise measured at the output of the PE3501. This indicates the PE3501 has a negligible affect on the phase noise of the system.

Figure 3. Phase Noise Plot


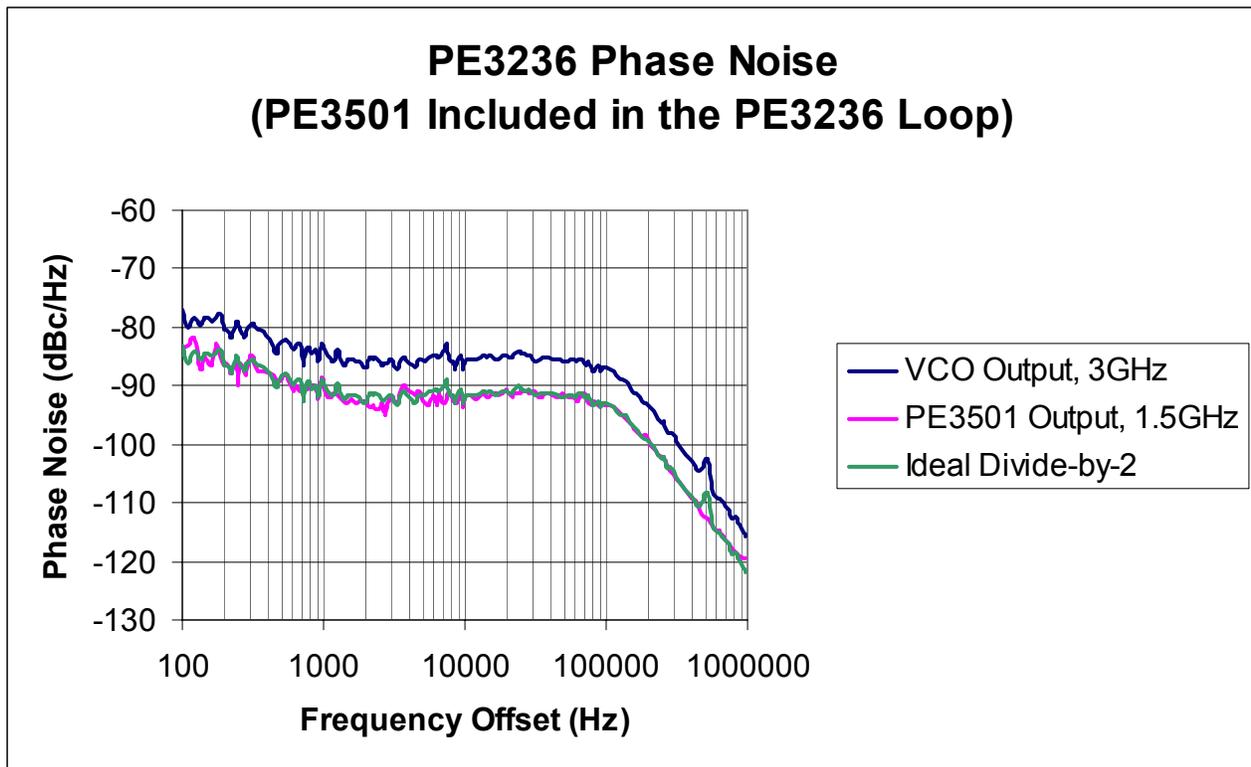


Figure 4. PE3236 / PE3501 Schematic

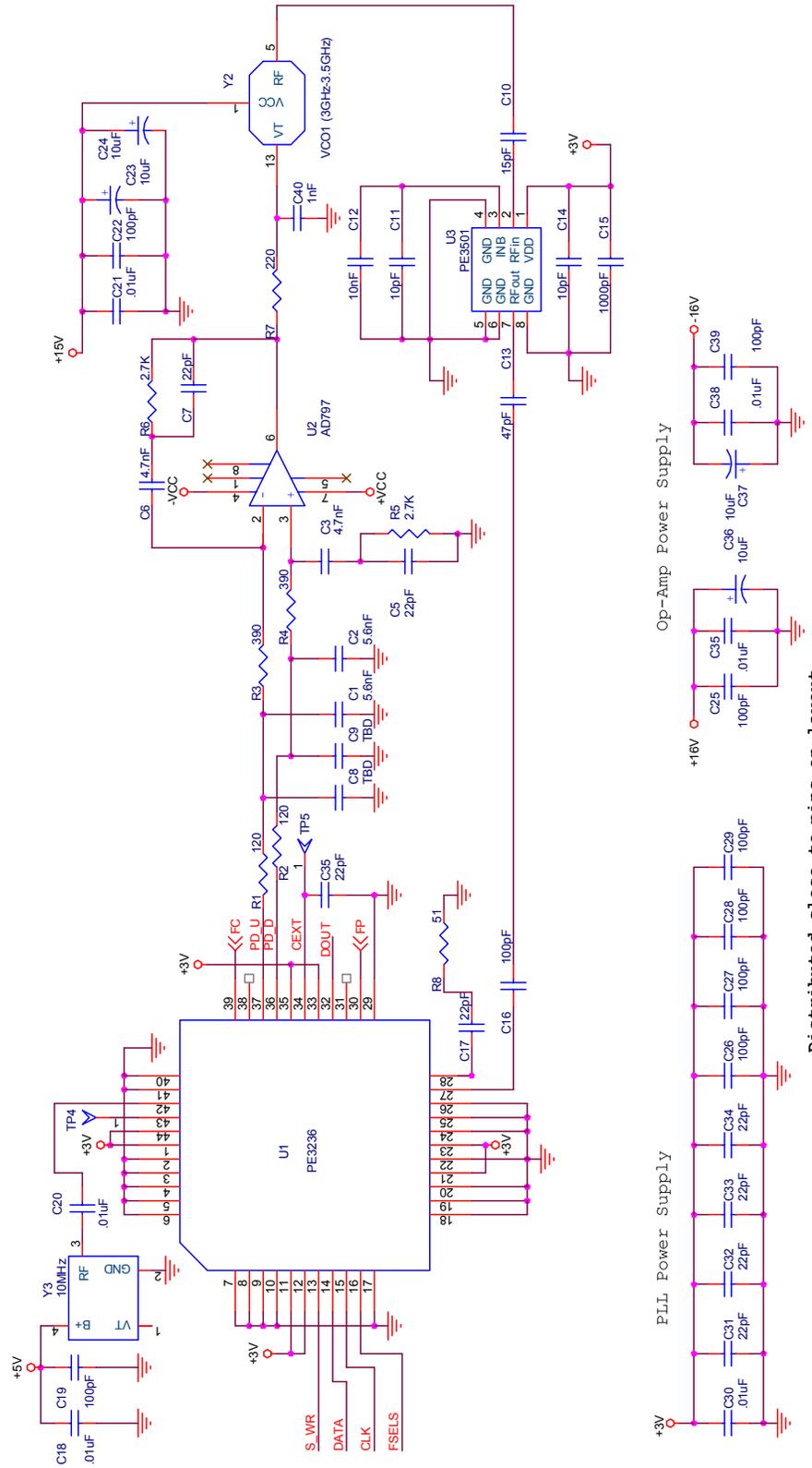

Sales Offices

United States

Peregrine Semiconductor Corp.

6175 Nancy Ridge Drive
San Diego, CA 92121
Tel 1-858-455-0660
Fax 1-858-455-0770

Japan

Peregrine Semiconductor K.K.

5A-5, 5F Imperial Tower
1-1-1 Uchisaiwaicho, Chiyoda-ku
Tokyo 100-0011 Japan
Tel: 03-3507-5755
Fax: 03-3507-5601

Europe

Peregrine Semiconductor Europe

Bâtiment Maine
13-15 rue des Quatre Vents
F- 92380 Garches
Tel 33-1-47-41-91-73
Fax 33-1-47-41-91-73

Australia

Peregrine Semiconductor Australia

8 Herb Elliot Ave.
Homebush, NSW 2140
Australia
Tel: 011-61-2-9763-4111
Fax: 011-61-2-9746-1501

For a list of representatives in your area, please refer to our Web site at: <http://www.peregrine-semi.com>

Application Note Identification

No patent rights or licenses to any circuits described in this application note are implied or granted to any third party.

Peregrine's products are not designed or intended for use in devices or systems intended for surgical implant, or in other applications intended to support or sustain life, or in any application in which the failure of the Peregrine product could create a situation in which personal injury or death might occur. Peregrine assumes no liability for damages, including consequential or incidental damages, arising out of the use of its products in such applications.

Peregrine products are protected under one or more of the following U.S. patents: 6,090,648; 6,057,555; 5,973,382; 5,973,363; 5,930,638; 5,920,233; 5,895,957; 5,883,396; 5,864,162; 5,863,823; 5,861,336; 5,663,570; 5,610,790; 5,600,169; 5,596,205; 5,572,040; 5,492,857; 5,416,043. Other patents may be pending or applied for.

*Peregrine, the Peregrine logotype, Peregrine Semiconductor Corp., and UTSi are registered trademarks of Peregrine Semiconductor Corporation.
Copyright © 2003 Peregrine Semiconductor Corp. All rights reserved.*